

CS-106

Mid-Semester Examination-I (Nov2024)
B.Tech. I Semester (CSE)
Electrical and Electronics Engineering

Duration: 1hr 30min

Max. Marks: 20

Note: Attempt all questions.

- Q1.a)** Define the following terms i)Active Element ii)Passive Element
iii)Independent Sources iv)Node v)Mesh [CO-1/5Marks]
OR

- b)** Using nodal analysis find the current flowing through 5 ohm resistance in fig.1.2 [CO-1/5 Marks]

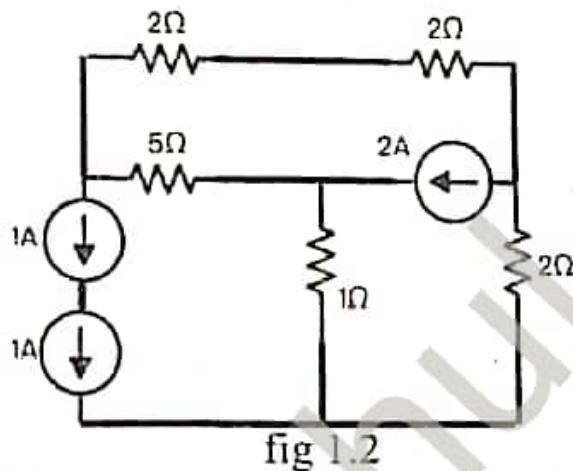


fig 1.2

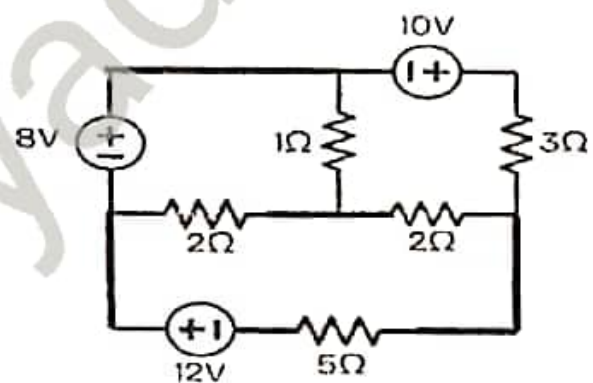


fig.2.1

- Q2.a)** Determine the current flowing in all resistances of the circuit shown in fig 2.1 using mesh analysis only [CO-1/5 Marks]
OR

- b)** In fig. 2.2 determine the current flowing through R_L when the value of load resistance R_L is i) 3 ohm, ii) 6 ohm & iii) 9 ohm [CO-1/5 Marks]

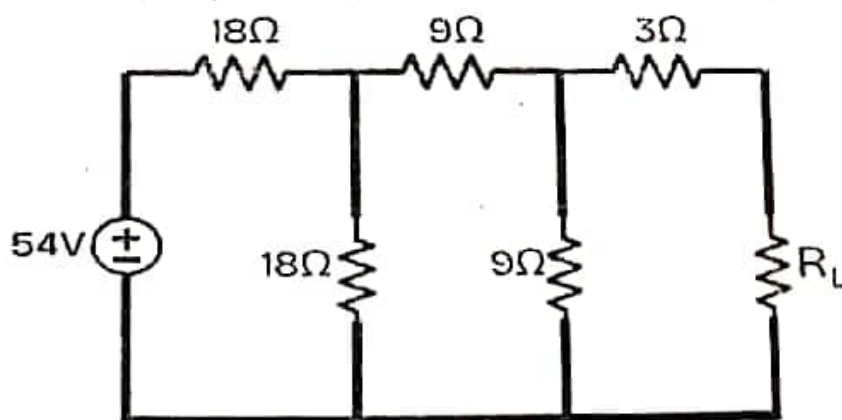


fig. 2.2

[1]

[P.T.O]