

LNCT UNIVERSITY

[Total No. of Questions: 4]

[Total No. of Printed pages: 1]

Enroll No.....

Class Roll No.....

First Mid Semester Examination, April 2024

DCES CS-203

Branch :CS Semester:2nd

Time 1:30 Hrs

Max. Marks 20

Note: All questions are compulsory.

Q.1 Write the equation using k map. $\Sigma (0, 2, 3, 6)$ & $d (5, 7)$ (CO 1 5marks)

OR

Q.1 Explain 3x8 Decoder with truth table and equations.

Q.2. Explain full Adder.

OR

(CO1 5marks)

Q.2. Explain serial adder.

Q.3. Explain SR Latch using NOR gate

(CO2 5 marks)

OR

Q.3 Distinguish between Transparent latch & Gated latch.

Q.4. Explain SR Flip Flop using NOR gate

(CO2 5 marks)

OR

Q.4 Explain the Latch input waveform. Which type of triggering used by Latches