

LNCT UNIVERSITY, BHOPAL

Enrollment No.

CS- 203**B.TECH I & II SEMESTER****EXAMINATION [DEC-2024]****DIGITAL CIRCUITS & EMBEDDED SYSTEMS**

Maximum Marks: 70

Time Allowed: 3 Hours

Note:- Attempt all questions. Internal choices are given.

(SECTION –A)**Q1 Short Answer Type Questions (Attempt Any Five) [5x6=30]**

- What are don't care conditions in Karnaugh maps? Explain with an example.
- Design a half subtractor and provide its truth table and Boolean expression.
- Explain the function of a carry look-ahead adder and its advantage over ripple carry adders.
- Describe the operation of a master-slave flip-flop with a neat diagram.
- What are races and hazards in asynchronous sequential circuits? How can they be mitigated?
- Discuss the various addressing modes of the 8051 microcontroller.
- Discuss the classification of embedded systems based on performance and functional requirements.

SECTION –B)**Q2. Long Answer Type Questions (Attempt Any Four) [4x10=40]**

- Design a 4-bit parallel binary adder using full adders and explain its working with a block diagram
- Design a synchronous 3-bit up-down counter using JK flip-flops. Provide the state diagram and timing diagram.
- Explain the working of an 8051 microcontroller, focusing on its architecture, registers, and instruction set.
- For a given asynchronous sequential circuit, the transition table is as follows. Perform state reduction and provide the new transition table.

Present State	Next State	Output
A	B	0
B	C	1
C	D	0
D	A	1
E	C	1

- Discuss the structure of embedded systems, comparing them with general-purpose computing systems. Include examples from different application areas.
- Write a basic assembly language program for the 8051 microcontroller to add two 8-bit numbers stored in registers R1 and R2, and store the result in register R0.