

LNCT UNIVERSITY, BHOPAL

EnrolmentNo..

CS-203UC

B.TECH (CS/AI ML) -I & II SEMESTER

EXAMINATION [JUNE-2024]

DIGITAL CIRCUITS & EMBEDDED SYSTEMS

Maximum Marks: 70

Time Allowed: 3 Hours

Note:- Attempt all questions internal choice are given.

(SECTION -A)**1. Short Answer Type Questions (Attempt Any Five) [5x6=30]**

- i. Obtain the minimal SOP expression for the following Boolean function using K-map and Implement the minimal SOP obtained using only NAND gates.

$$F(w,x,y,z) = \sum m(0,1,5,9,13,14,15) + \sum d(3,4,7,10,11)$$
- ii. Design a full adder using Multiplexer
- iii. Write the characteristic, excitation tables for JK, RS, T and D flip-flops.
- iv. Design 4 bit PISO Shift Register.
- v. What is critical and non-critical races in asynchronous circuits? How to avoid races?
- vi. Explain about analysis procedure in sequential circuits in detail.
- vii. Explain the Interrupt Structure with the associated register in 8051 microcontroller.
- viii. Explain the Interfacing of Keyboard/Display with 8051 microcontroller.

(SECTION -B)**2 Long Answer Type Questions (Attempt Any Four) [04x10=40]**

- i. Design a 4 bit parallel adder using Full adder modules.
- ii. Explain the term Race around condition. How is it satisfied by Master-slave Flip-Flops?
- iii. Using D-Flip flops and waveforms, explain the working of a 4-bit SISO shift register.
- iv. Implement the switching function

$$F = \sum m(1, 3, 5, 7, 8, 9, 14, 15)$$
 by a static hazard free two level AND- OR network.
- v. Explain the data transfer instructions of timer unit in 8051 microcontroller.
- vi. Convert SR flip flop to T flip flop.